 


# Accurate charge measurement of fast signals via FPGA\* based TDC's

Wolfgang Koenig, Jerzy Pietraszko, Michael Traxler

Joint venture of the Hades Collaboration & the Dep. of Experiment-Elektronik @ GSI



## Menu:


- Concept
- Amplifier
- Integrator
- First results
- Application for HADES Veto detector
- New FPGA based TDC concept
- First Results
- Summary & outlook



\*Field Programmable Gate Array (AND/Or/Not Logic + FlipFlops + fancy interfaces + ... )
 
# The basic concept:


general purpose (Driftchambers, straw tubes, PM's, Diamonds)



keep it **s**mall and **s**imple  
Minimum: 2 resistors, 1 capacitor




Complex **c**ommercial **e**lement

come & kiss

 
   
## Fast amplifier




- Low noise: Noise figure: **0.5@1.8GHz**
- Rise time: **240 ps** (100 ps input)
- Fall time: **210 ps** (100ps input)
- Transition frequency: **42 GHz**
- Voltage Gain: **20** (50 Ohm in, 100 Ohm out)



Integrated Noise

Output: (V rms)  
3,0871E-4

## Simple-most integrator

   


**High sensitivity (high gain) for low frequencies:**  
 low frequency noise dominates resolution  
**Not** a spectroscopy amplifier

### Advantage:



- Short cycle time  $\sim 50$  ns  $\rightarrow$  High rate capability
- Triggered baseline-restorer: no rate dependent trigger threshold due to triggered feedback
 
# Simulation with discrete components

Risetime: **1ns**  
Fall time: **5ns**  
Pulse height:  
**Top: 0.25mA**  
**Bottom: 1.5 mA**







  Non-linear amplifier response,  
dynamic range about 10 -100  
depending on signal width



# Prototype Board (4 channels) for TRB 2

73 mm

    

Size determined by connectors and TRB 2 infrastructure

## First Results



Pulser  $t_{\text{rise}} = 1.5\text{ns}$  ,  $t_{\text{fall}} = 2.5\text{ ns}$

Large jitter of the integrator width (charge)  
Due to high gain for low frequency noise

After walk correction via leading edges:  
Charge Resolution: **0.17 %**


Calorimeter  $\leq 0.1\%$  @ 1GeV  
excluding detector performance,  
educated guess

  Resolution scales roughly  
like  $\text{Sqrt}(\text{charge})$





Veto (monocrystalline diamond, 100 um thickness,  $8.5 * 8.3 \text{ mm}^2$ , 16 x-, 16 y-strips)

 Limited dynamic range: factor 10  
Resolution: 0.5% in charge (to be verified)




Resolution sufficient to separate Z from Z+1  
even up to Uranium (2%)

**Radiation Damage ?**

  
 
# TDC in FPGA: Theory


- Developed, implemented and tested in hardware by Eugen Bayer
- The used method is very simple! **Tapped Delay Line**
  - The asynchronous input signal (e.g. one rising edge) runs through a chain of delay elements
  - The position of the 0/1 transition is stored in the FF array at the next rising edge of the system clock



**Medium size FPGA: several 10000 flip-flops + logic elements**
 
# TDC in FPGA (II): Reality

- The "Carry-Chain" serves as a delay chain
- Carry-Chain multiplexers are the delay elements
- Delay (max.) = 45 ps (Virtex-4: CIN to COUT = 90 ps)
- Real delays vary: cell-by-cell calibration necessary




## Consequences:

- Bad Differential Non Linearity (DNL) needs calibration (in FPGA or offline)
- Trick to improve resolution: measure several times to "remove" ultra wide bins
 
# TDC in FPGA : Architecture for Multi-Hit capability

- TDL method extended with “Wave Union” method
- Pipelined design
- Dead time = 15 ns (3 sys-clock cycles)
- Buffer for 512 hits per channel





# TDC in FPGA : Results

- TDC time resolution down to 3.6 ps RMS
- No tails
- World record!
- For a large number of channels: RMS ~ 10ps

- Temperature dependence: **8 ps / K**
- Voltage: ~4 ps for 10 mV supply voltage change
- **Needs load balancing via dummy activities**
- No crosstalk measured (proper PCB design)
- Up to 56 channels on XC4VLX40 with 40k logic cells

**FPGA in TDC works extremely well!**

 

 

- 4 modern FPGA-TDCs with high pin count (208) connectors (add on boards)
- Low noise power supply (48V)
- Network: 8 times up to 3Gbit/s and/or 1Gbit/s Ethernet

# Hades & the KISS principle

## Electronics

- 4,500 PCB's in total
- 1,500 ADC channels (multiplexed from 80,000 signals)
- 30,000 TDC channels

## Data Rates:


- Up to 100 kHz trigger rate
- 250 MByte/s (average), 400 MByte/s (peak)

## Data transport

- 550 FPGA's
- 1050 optical transceivers
- 7,000 m optical fibre
- 800 m 1-wire & CAN bus
- 32 Ethernet switches
- 15 Gbit/s uplink to Eventbuilders
- 10 Gbit/s uplink to storage
 
## Server farm

- 160 TB hard disks
- 44 CPU cores
- 100 TB storage / week via Robot



Many elements (~100) / subsystem

# Summary & outlook

## Summary:

- New concept for measuring charge with high resolution TDC.
- High rate capability (several MHz)
- New concept for implementing TDC's in FPGA's
- Promising first results
- Not yet there

## Outlook:

- Include more of the FEE inside the FPGA:
  - ◆ Discriminators → LVDS receivers
  - ◆ DAC's → integrated logic pulses with variable duty cycle
- Test with real diamond signals in beam

On the way

